

Technical University of Munich

Neuroprosthetics Exercise 2 Report

Student Name: Abdelrahman Elsisy

Student Number: 03780605



1. SLOPE FIELDS

The equations given contain a function and its derivative, therefore, they are referred to as differential equations. A derivative of a function gives you slopes at different points of a plane. For example, equation (1) below gives the slope at each point in the (x,y) plane. In the exercise, we are given equations (2) and (3) below. The equations show the rate of change of Voltage (volts) over time (seconds) with respect to voltage and time. To obtain an isocline we set the derivative or slope to a specific value. For equation 1 we are given the set of slope values [-3 V/s, -1 V/s and 1 V/s] and for equation 2 we are given the set of slope values [-2 V/s, 0 V/s and 2 V/s]. **Figures 1 and 2** illustrate the plotted slope fields of equations (2) and (3) with their isoclines respectively.

$$y' = f(x,y) \quad (1)$$

$$\frac{dV}{dt} = -10 - V - t \quad (2)$$

$$\frac{dV}{dt} = \cos(t) - \frac{1}{2}V + 20 \quad (3)$$

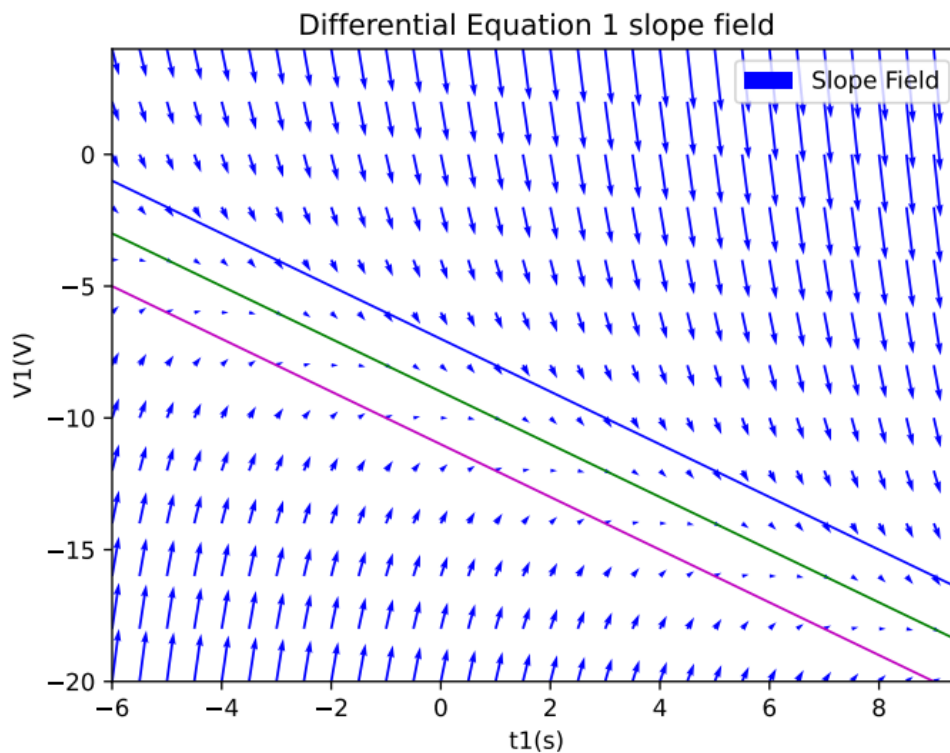


Figure 1. Slope Field and Isoclines of equation 1

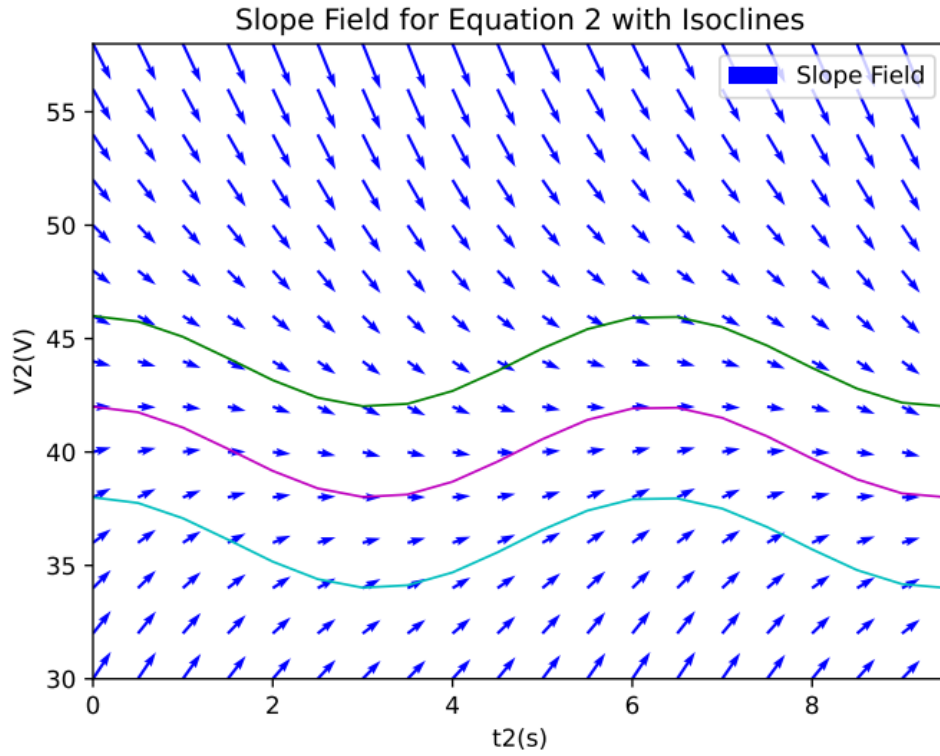


Figure 2. Slope Field and Isoclines of equation 2

2. SIMPLE CELL MODEL

As per discussed in the lecture, a simple circuit of a cell can be represented as an R-C circuit. The circuit given in the exercise consists of a current source (I_{ex}), and a resistor (R_l) and a capacitor (C_m) connected together in **parallel**. If two electrical components are connected together in parallel then the total current is divided over the two electrical components. Hence, we obtain equations (4). After substituting the value of (I_{ex}) given in equation (5) we obtain equation (6). After making the slope (dV/dt) the subject and simplifying the equation we obtain equation (7).

$$I_{ex} = C_m \frac{dV}{dt} + \frac{V}{R_l} \quad (4)$$

$$I_{ex} = I_{max} \cdot \sin(t) \quad (5)$$

$$I_{max} \cdot \sin(t) = C_m \frac{dV}{dt} + \frac{V}{R_l} \quad (6)$$

$$\frac{dV}{dt} = \frac{1}{C_m} (I_{max} \cdot \sin(t) - \frac{V}{R_l}) \quad (7)$$

2.1. PLOTTED SLOPE FIELDS

a) **Figures 3** show the plotted slope fields for equation (7) given the following parameters respectively:

- $R_{l1} = 1 \text{ Ohm}; C_{m1} = 2 \text{ F}; I_{\max1} = 0 \text{ A}$
- $R_{l2} = 1 \text{ Ohm}; C_{m2} = 2 \text{ F}; I_{\max2} = 10 \text{ A}$

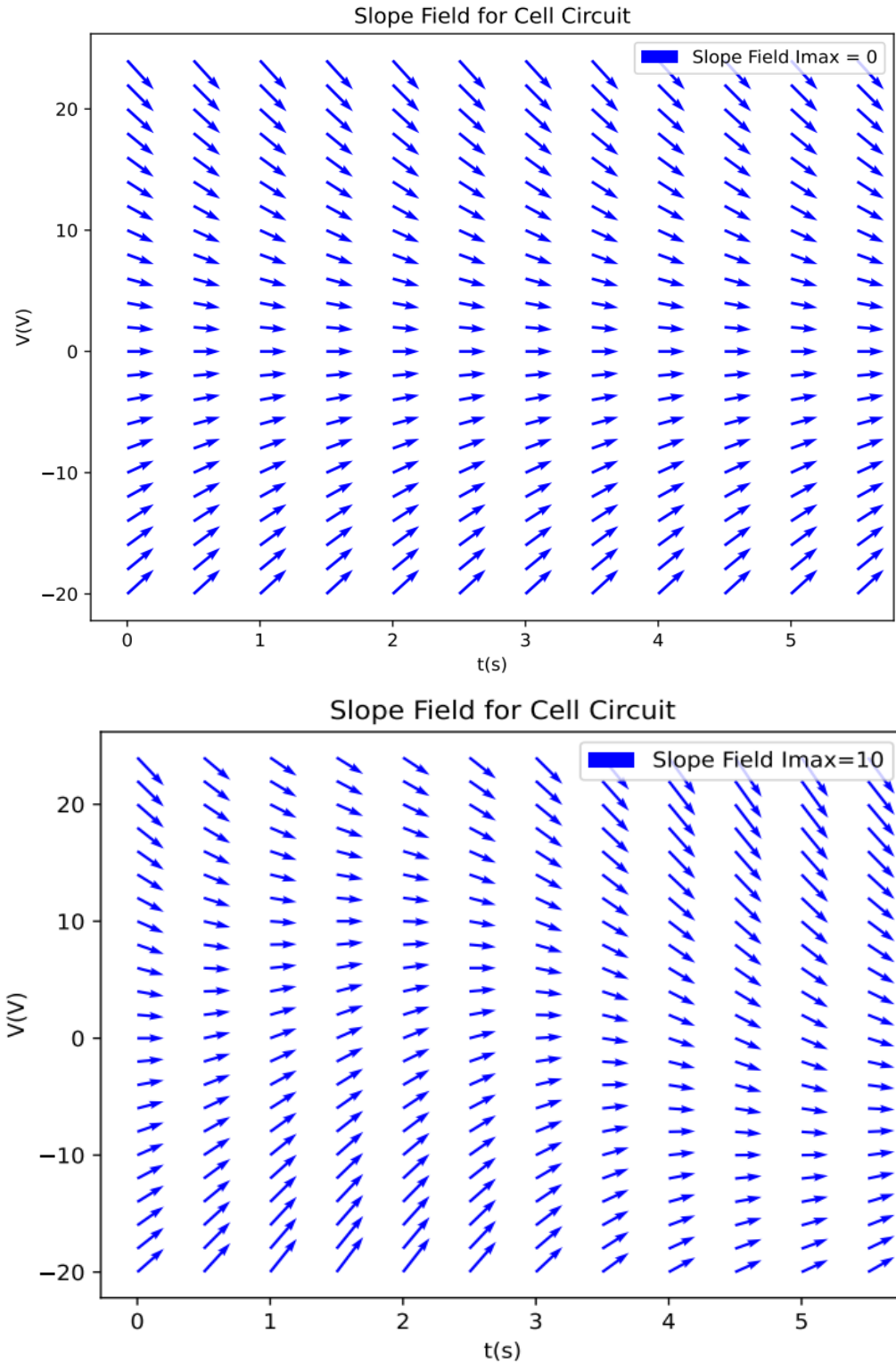


Figure 3. Slope fields for the equation derived from the cell equivalent circuit. Top: $R_{l1} = 1 \text{ Ohm}; C_{m1} = 2 \text{ F}; I_{\max1} = 0 \text{ A}$. Bottom: $R_{l2} = 1 \text{ Ohm}; C_{m2} = 2 \text{ F}; I_{\max2} = 10 \text{ A}$

b) Now after we add a constant term $D = 5 \text{ A}$ to the current source, we obtain equation (8) for the total current. Then we substitute the value of I_{ex} with the value given in equation (5) and obtain equation (9). After making the slope (dV/dt) the subject and simplifying the equation we obtain equation (10). Figures 4 and 6 show the plotted slope fields for equation (7) given the following parameters respectively.

- $R_{l1} = 1 \text{ Ohm}; C_{m1} = 2 \text{ F}; I_{max1} = 0 \text{ A}$
- $R_{l2} = 1 \text{ Ohm}; C_{m2} = 2 \text{ F}; I_{max2} = 10 \text{ A}$

$$I_{ex} + D = C_m \frac{dV}{dt} + \frac{V}{R_l} \quad (8)$$

$$I_{max} \cdot \sin(t) + D = C_m \frac{dV}{dt} + \frac{V}{R_l} \quad (9)$$

$$\frac{dV}{dt} = \frac{1}{C_m} (I_{max} \cdot \sin(t) + D - \frac{V}{R_l}) \quad (10)$$

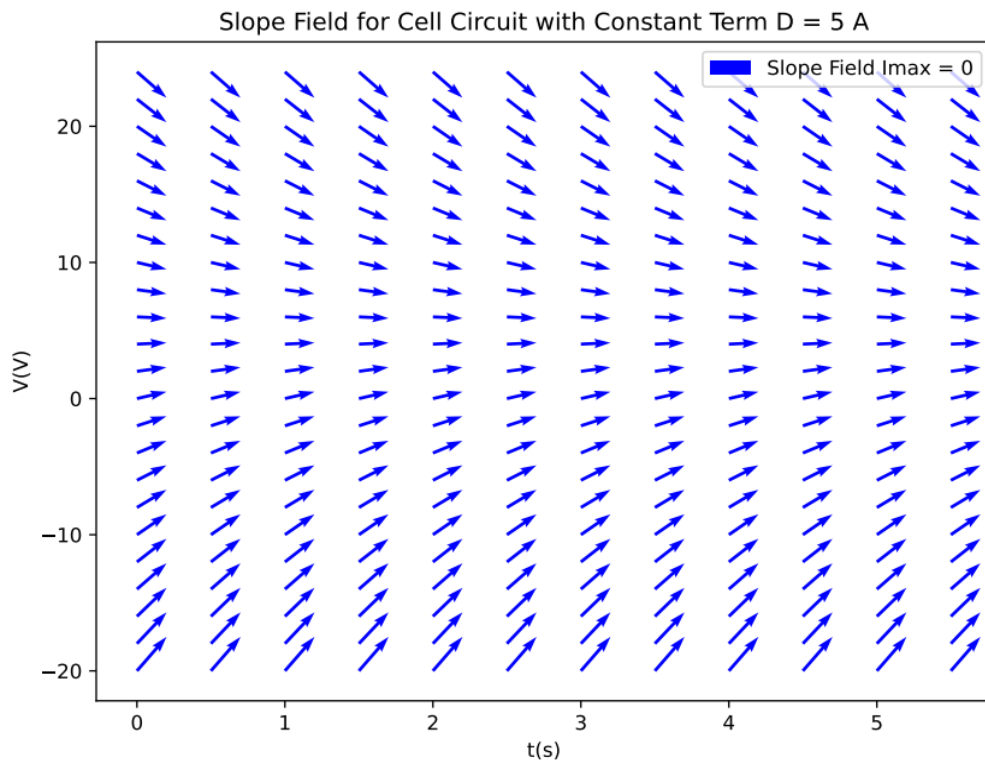


Figure 4. Slope field for the equation derived from the cell equivalent circuit with constant term $D = 5 \text{ A}$.
Top: $R_{l1} = 1 \text{ Ohm}; C_{m1} = 2 \text{ F}; I_{max1} = 0 \text{ A}$.

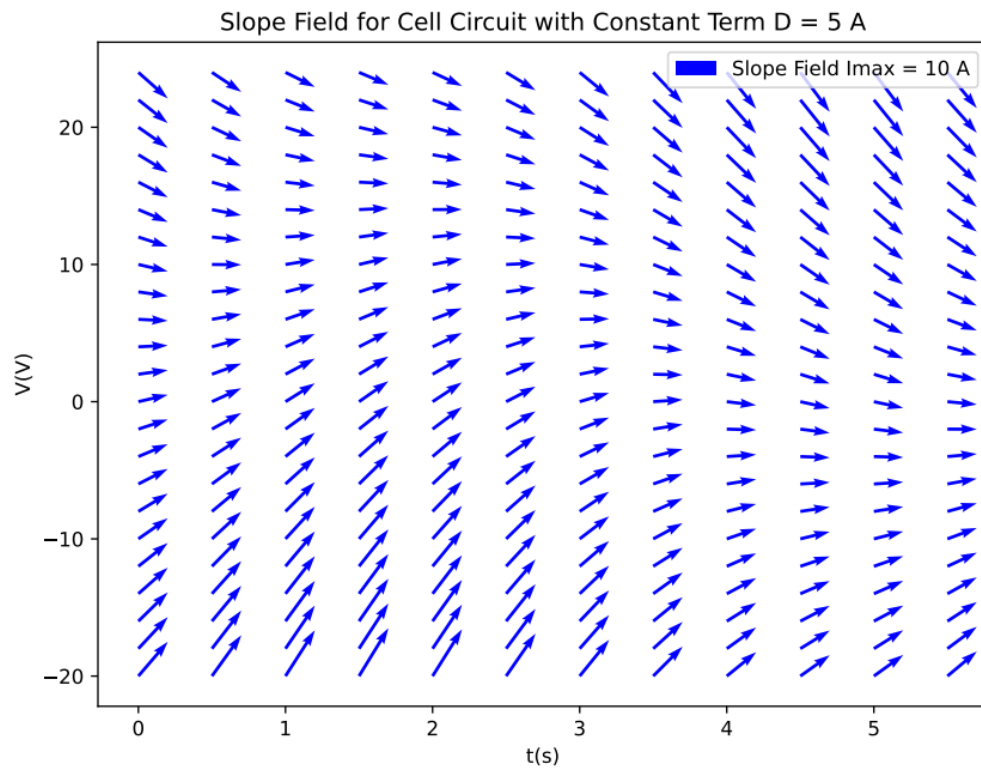


Figure 5. Slope field for the equation derived from the cell equivalent circuit with constant term $D = 5$ A.
Top: $R_{l1} = 1$ Ohm; $C_{m1} = 2$ F; $I_{max2} = 10$ A.